

5 – RLT and Verilog Review

ECE 474A/574A
COMPUTER-AIDED LOGIC DESIGN

RTL Design Method


2

Step		Description
Step 1:	Capture the high-level FSM	Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is "high-level" because the transition conditions and the state actions are more than just Boolean operations on bit inputs and outputs
Step 2:	Create a datapath	Create a datapath to carry out the data operations on the high-level state machine
Step 3:	Connect the datapath to the controller	Connect the datapath to the controller block. Connect external Boolean inputs and output to the controller block
Step 4:	Derive the controller's FSM	Convert the high-level state machine to a finite-state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath

Laser-Based Distance Measurer

Step 1: Capture a high-level state machine

3

 


- ❑ Example of how to create a high-level state machine to describe desired processor behavior
- ❑ Laser-based distance measurement – pulse laser, measure time T to sense reflection
 - ❑ Laser light travels at speed of light, $3 * 10^8 \text{ m/sec}$
 - ❑ Distance is thus $D = T \text{ sec} * 3 * 10^8 \text{ m/sec} / 2$

Laser-Based Distance Measurer

Step 1 : Capture a high-level state machine

4

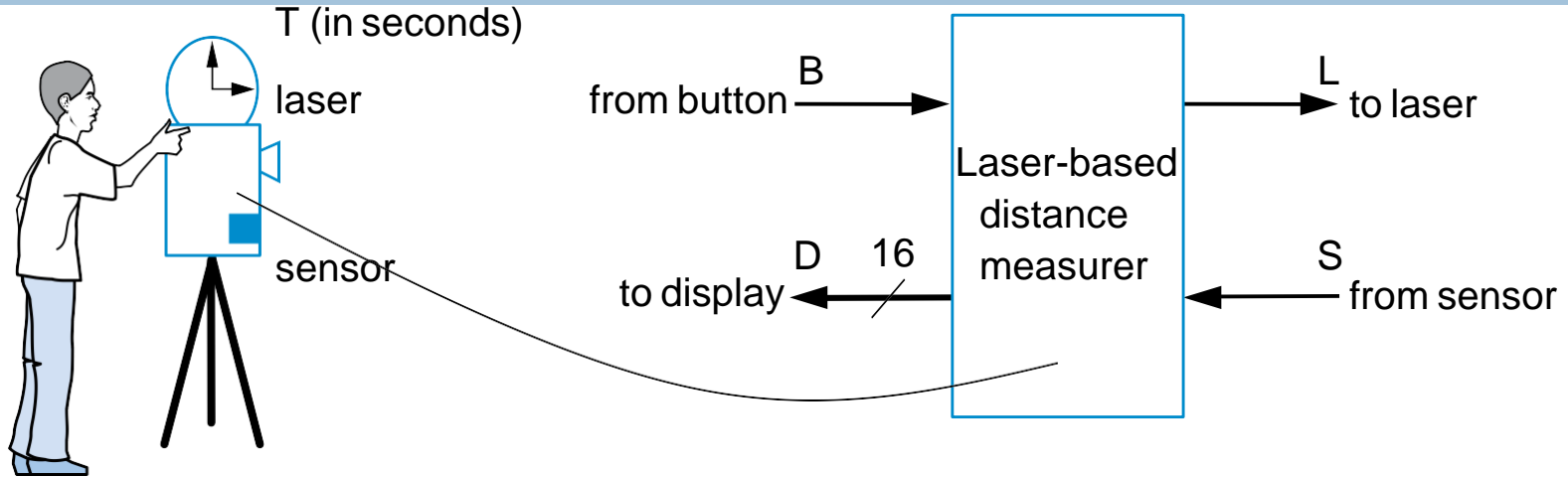

Inputs/outputs

- ▣ B : bit input, from button to begin measurement
- ▣ L : bit output, activates laser
- ▣ S : bit input, senses laser reflection
- ▣ D : 16-bit output, displays computed distance



Laser-Based Distance Measurer

Step 1 : Capture a high-level state machine

5

Inputs: B, S (1 bit each)

Outputs: L (bit), D (16 bits)

  

- ▣ Step 1: Create high-level state machine
- ▣ Begin by declaring inputs and outputs
- ▣ Create initial state, name it **S0**
 - ▣ Initialize laser to off (L=0)
 - ▣ Initialize displayed distance to 0 (D=0)



Laser-Based Distance Measurer

Step 1 : Capture a high-level state machine

6

Inputs: B, S (1 bit each)

Outputs: L (bit), D (16 bits)

  

- Add another state, call **S1**, that waits for a button press
 - B' – stay in **S1**, keep waiting
 - B – go to a new state **S2**

Q: What should S2 do?



A: Turn on the laser

Laser-Based Distance Measurer

Step 1 : Capture a high-level state machine

7

  Inputs: B, S (1 bit each)
Outputs: L (bit), D (16 bits)



- Add a state **S2** that turns on the laser (L=1)
- Then turn off laser (L=0) in a state **S3**

Q: What should the next state do?



A: Start timer, wait to sense reflection

Laser-Based Distance Measurer

Step 1 : Capture a high-level state machine

8

  Inputs: B, S (1 bit each)
Outputs: L (bit), D (16 bits)
Local Registers: Dctr (16 bits)





- Stay in **S3** until sense reflection (S)
- To measure time, count cycles for which we are in **S3**
 - To count, declare local register *Dctr*
 - Increment *Dctr* each cycle in **S3**
 - Initialize *Dctr* to 0 in **S1**. **S2** would have been O.K. too

Laser-Based Distance Measurer

Step 1 : Capture a high-level state machine

9

  Inputs: B, S (1 bit each)
Outputs: L (bit), D (16 bits)
Local Registers: Dctr (16 bits)



- Once reflection detected (S), go to new state **S4**
 - Calculate distance
 - Assuming clock frequency is 3×10^8 , *Dctr* holds number of meters, so $D = Dctr / 2$
- After **S4**, go back to **S1** to wait for button again

Laser-Based Distance Measurer

Step 2: Create a Datapath

10

- Datapath must
 - ▣ Implement data storage
 - ▣ Implement data computations

- Look at high-level state machine, do three substeps
 - a) Make data inputs/outputs be datapath inputs/outputs
 - b) Instantiate declared registers into the datapath (also instantiate a register for each data output)
 - c) Examine every state and transition, and instantiate datapath components and connections to implement any data computations

Instantiate: to introduce a new component into a design.

Laser-Based Distance Measurer

Step 2: Create a Datapath


11

- Make data inputs/outputs be datapath inputs/outputs
- Instantiate declared registers into the datapath (also instantiate a register for each data output)
- Examine every state and transition, and instantiate datapath components and connections to implement any data computations

Inputs: B, S (1 bit each)

Outputs: L (bit), D (16 bits)

Local Registers: Dctr (16 bits)

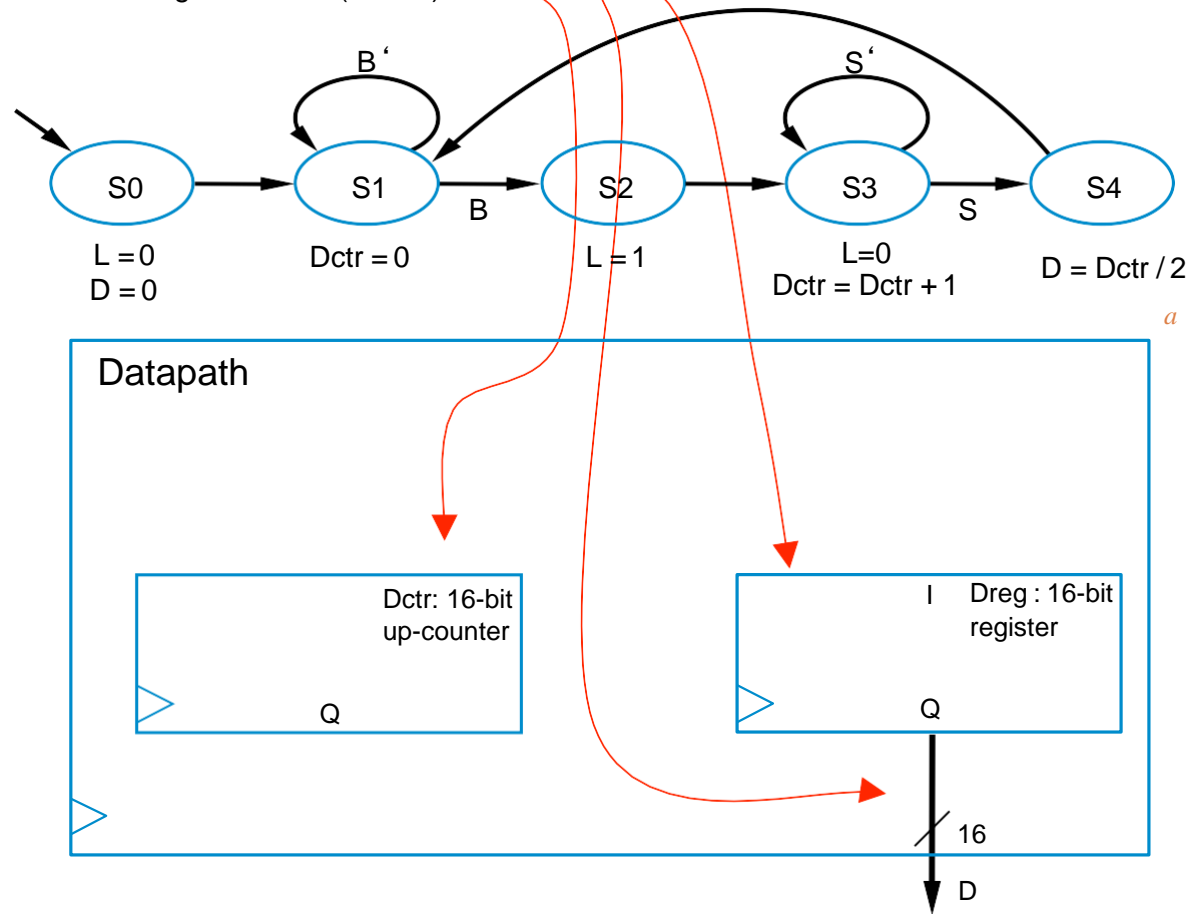

Laser-Based Distance Measurer

Step 2: Create a Datapath



12

- Make data inputs/outputs be datapath inputs/outputs
- Instantiate declared registers into the datapath (also instantiate a register for each data output)
- Examine every state and transition, and instantiate datapath components and connections to implement any data computations

Inputs: B, S (1 bit each)

Outputs: L (bit), D (16 bits)


Local Registers: Dctr (16 bits)

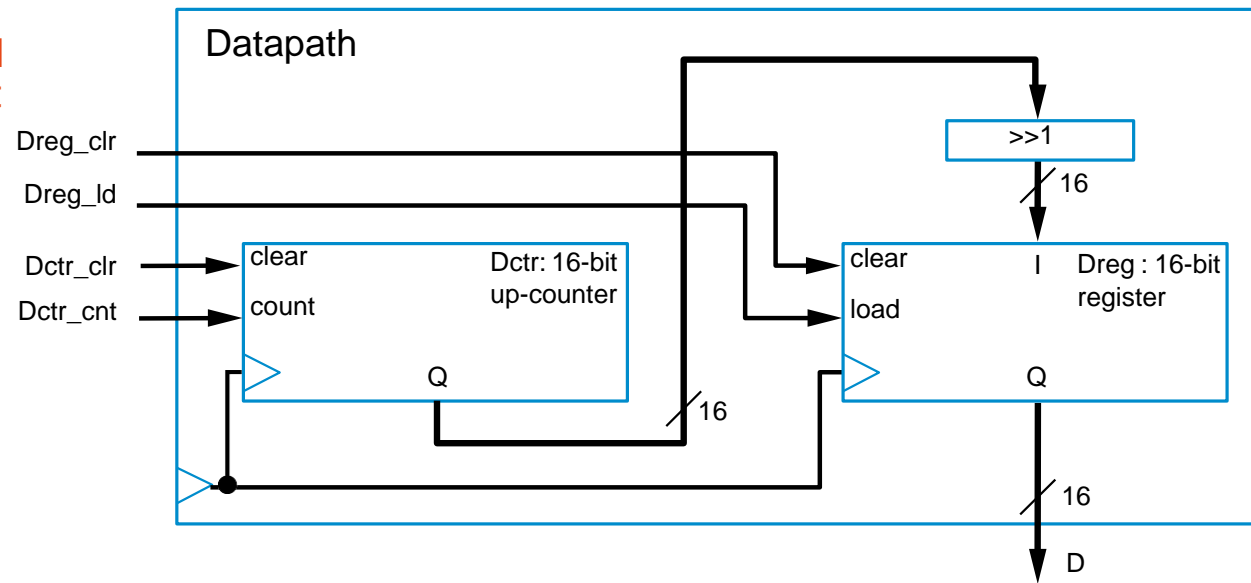 


Laser-Based Distance Measurer

Step 3: Connect datapath to controller

13

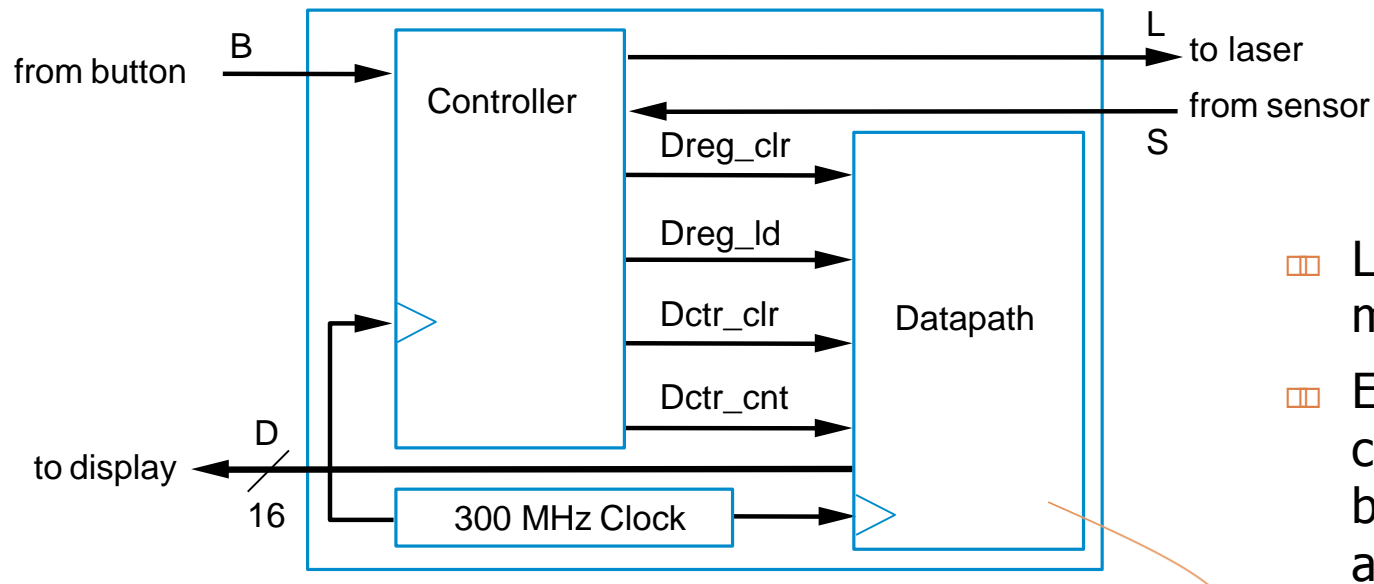

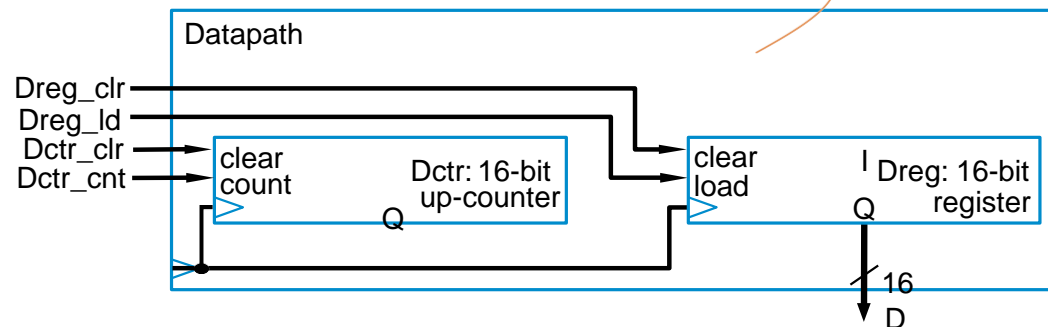- ▣ Laser-based distance measurer example
- ▣ Easy – just connect all control signals between controller and datapath





Laser-Based Distance Measurer

Step 4: Derive controller's FSM


14

FSM has same structure as high-level state machine

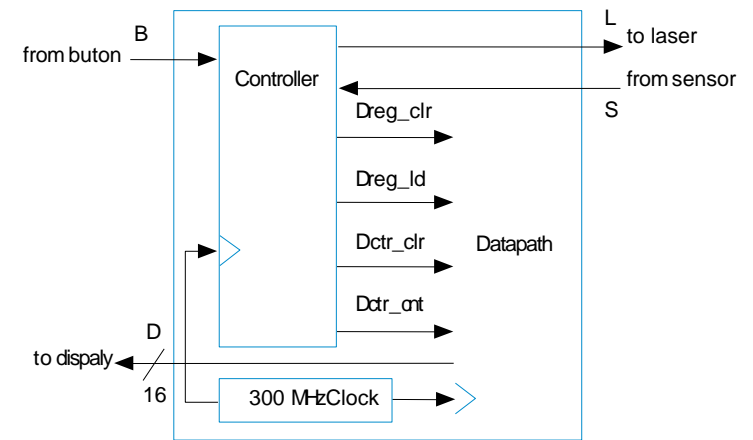 - Inputs/outputs all bits now
- Replace data operations by bit operations using datapath



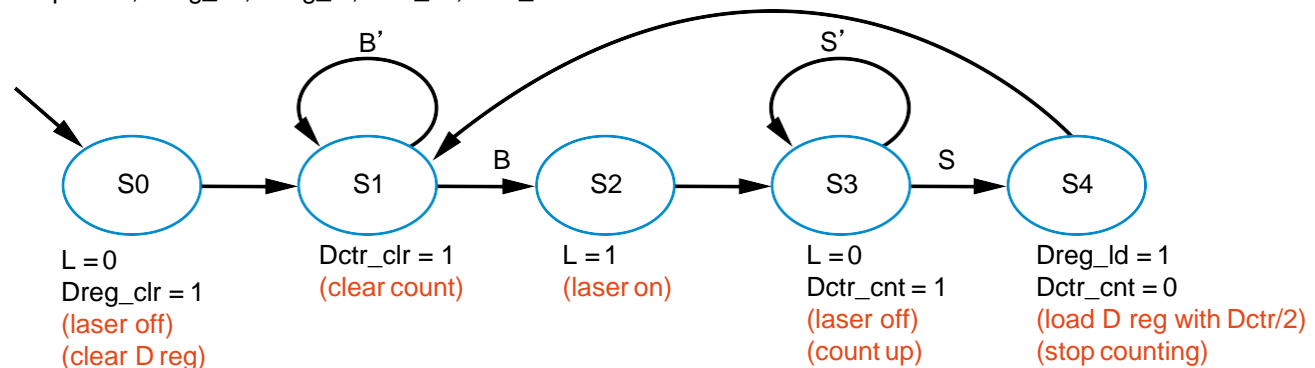
Inputs: B, S
Outputs: L, Dreg_clr, Dreg_ld, Dctr_clr, Dctr_cnt



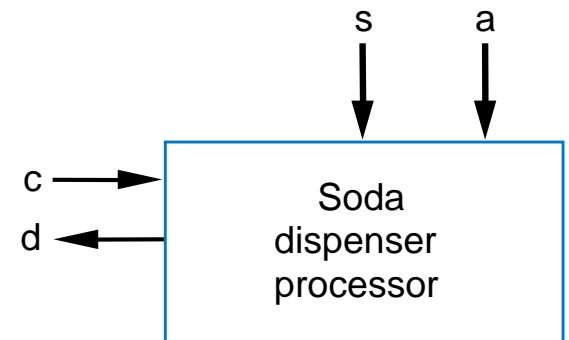Exercise



Using the RTL design process, design a soda dispenser with the following characteristics

- c*: bit input, 1 when coin deposited
- a*: 8-bit input having value of deposited coin
- s*: 8-bit input having cost of a soda
- d*: bit output, processor sets to 1 when total value of deposited coins equals or exceeds cost of a soda





HLSM Timing

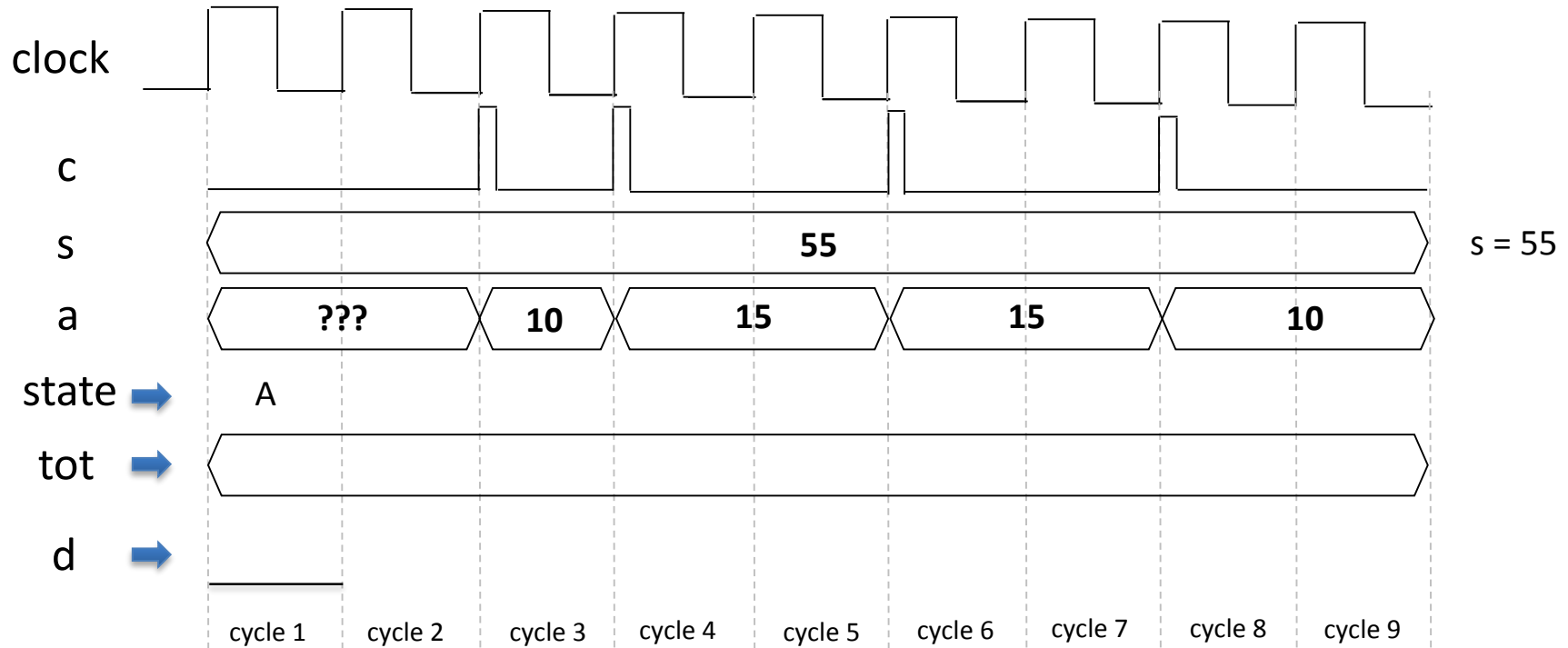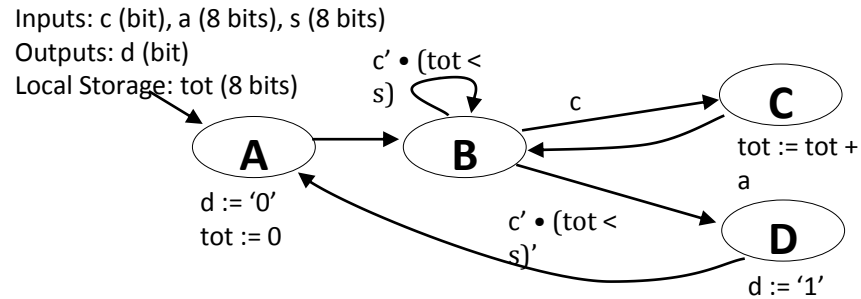

Treadmill example




Exercise

 1. What is the value of D in state K?
a. 7; b) 9; c) 12; d) 15; e) none of the above
2. Design the datapath and controller for the following HLSM

Outputs: X (8-bits), Y (8-bits)

Local Storage: X (8-bits), Y (8-bits), D (8-bits)




High-Level State Machine Behavior


15

- Register-transfer level (RTL) design captures desired system behavior using high-level state machine
 - Earlier example – 3 cycles high, used FSM
 - What if 512 cycles high? 512-state FSM?
 - Better solution – High-level state machine that uses register to count cycles
 - Declare explicit register Cnt (2 bits for 3-cycles high)
 - Initialize Cnt to 2 (2, 1, 0 → 3 counts)
 - "On" state
 - Sets $X=1$
 - Configures Cnt for decrement on next cycle
 - Transitions to Off when Cnt is 0
 - Note that transition conditions use current value of Cnt, not next (decremented) value
 - For 512 cycles high, just initialize Cnt to 511

Inputs: B; Outputs: X

 

Inputs: B; Outputs: X; Register: Cnt(2)

 

High-Level State Machine Behavior

16

- ▣ Module ports same as FSM
- ▣ Same two-procedure approach as FSM
 - ▣ One for combinational logic, one for registers
 - ▣ Registers now include explicit registers (**Cnt**)
 - ▣ Two reg variables per explicit register (**current** and **next**), just like for state register

```

`timescale 1 ns/1 ns

module LaserTimer(B, X, Clk, Rst);


    input B;
    output reg X;
    input Clk, Rst;

    parameter S_Off = 0,
              S_On  = 1;

    reg [0:0] State, StateNext;
    reg [1:0] Cnt, CntNext;

    // CombLogic
    always @(State, Cnt, B) begin
        ...
    end

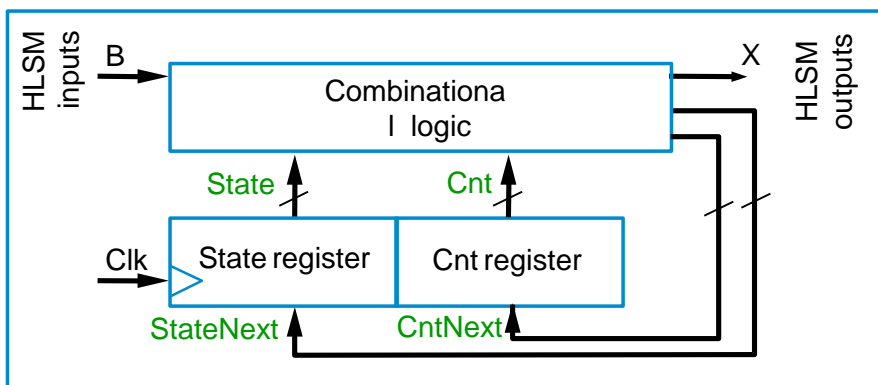    // Regs
    always @(posedge Clk) begin
        ...
    end
endmodule
    
```





High-Level State Machine Behavior

17

- CombLogic process
 - Describes actions and transitions

Inputs: B; Outputs: X; Register: Cnt(2)

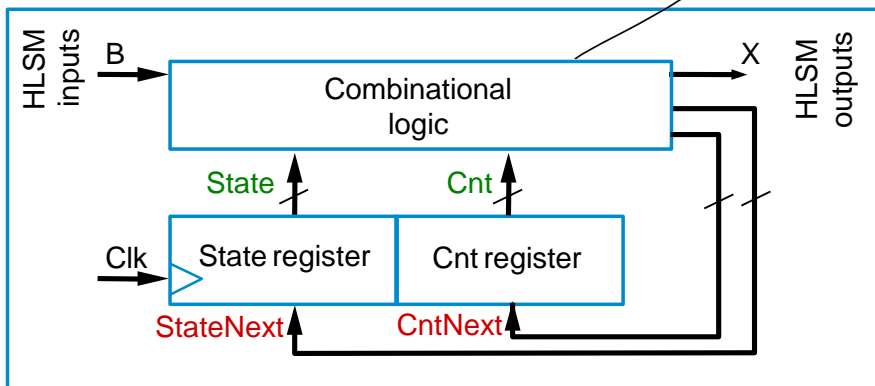 

```
...
reg [0:0] State, StateNext;
reg [1:0] Cnt, CntNext;

// CombLogic
always @(State, Cnt, B) begin
    case (State)
        S_Off: begin
            X <= 0;
            CntNext <= 2;
            if (B == 0)
                StateNext <= S_Off;
            else
                StateNext <= S_On;
        end
        S_On: begin
            X <= 1;
            CntNext <= Cnt - 1;
            if (Cnt == 0)
                StateNext <= S_Off;
            else
                StateNext <= S_On;
        end
    endcase
end
...
```

Note: Writes are to "next" variable, reads are from "current" variable. See target architecture to understand why.



High-Level State Machine Behavior

18

Regs process

- Updates registers on rising clock

Inputs: B; Outputs: X; Register: Cnt(2)

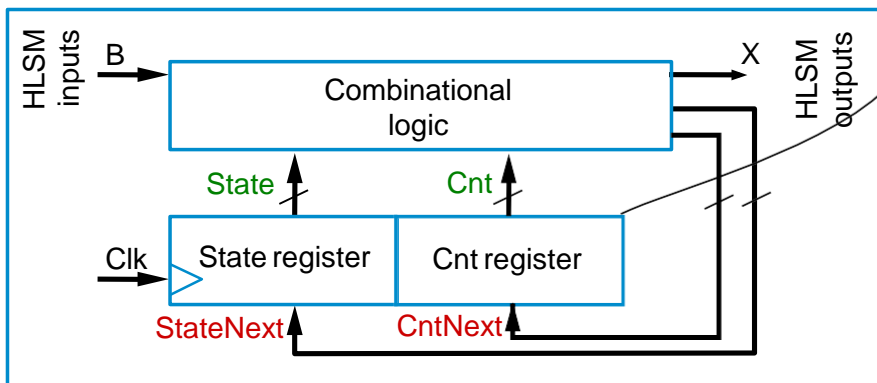 



```
...
// Regs
always @(posedge Clk) begin
    if (Rst == 1 ) begin
        State <= S_Off;
        Cnt <= 0;
    end
    else begin
        State <= StateNext;
        Cnt <= CntNext;
    end
end
...
```


Top-Down Design: HLSM to Controller and Datapath

19

Deriving a datapath from the HLSM

Inputs: B; Outputs: X; Register: Cnt(2)

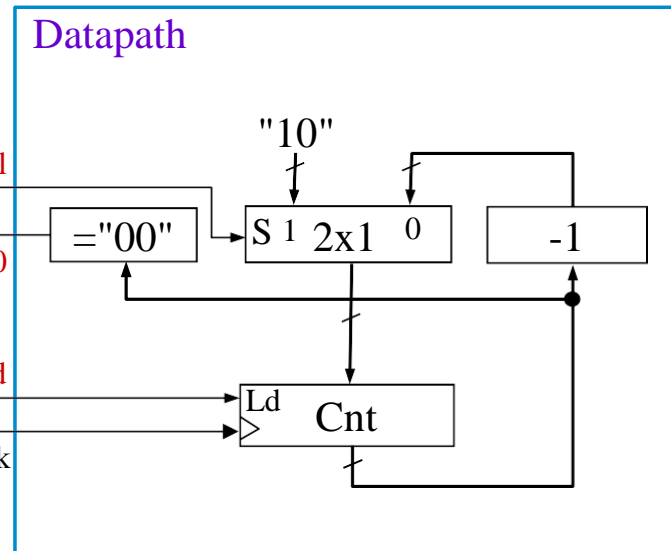 


Top-Down Design: HLSM to Controller and Datapath

20



Deriving a controller

- Replace HLSM by FSM that uses the datapath

Inputs: B; Outputs: X; Register: Cnt(2)

 

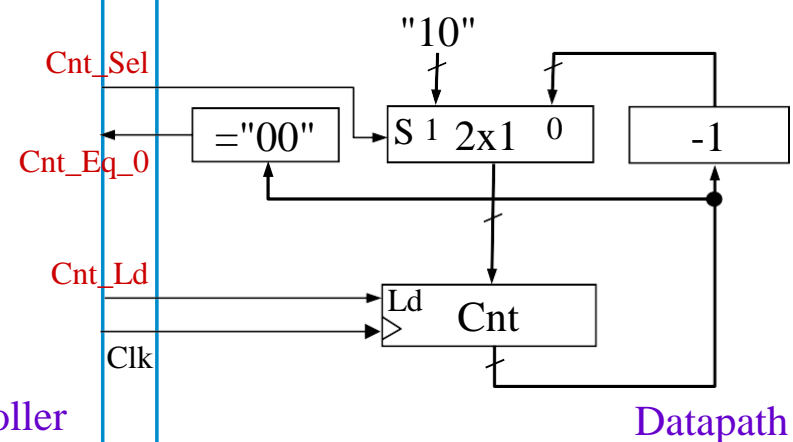 
Inputs: B, Cnt_Eq_0; Outputs: X, Cnt_Sel, Cnt_Ld;



Top-Down Design: HLSM to Controller and Datapath

21

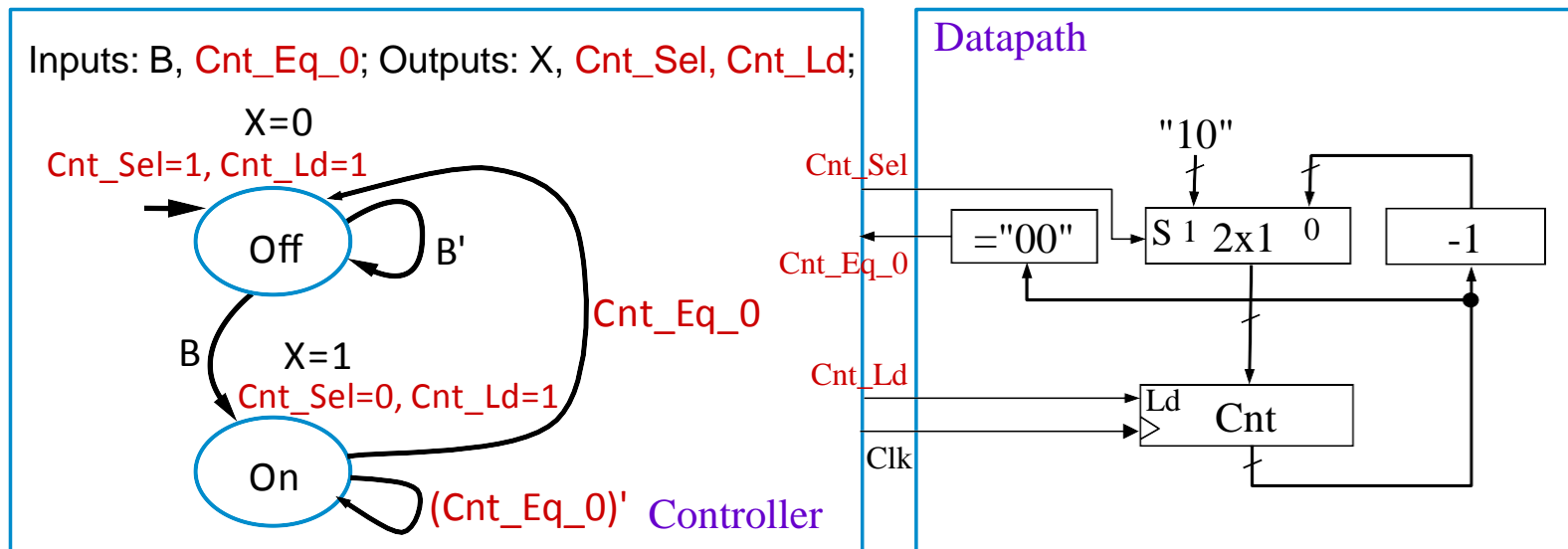- Describe controller and datapath in VHDL
 - One option: structural datapath, behavioral (FSM) controller
 - Let's instead describe both behaviorally




Describing a Datapath Behaviorally

22

Two procedures

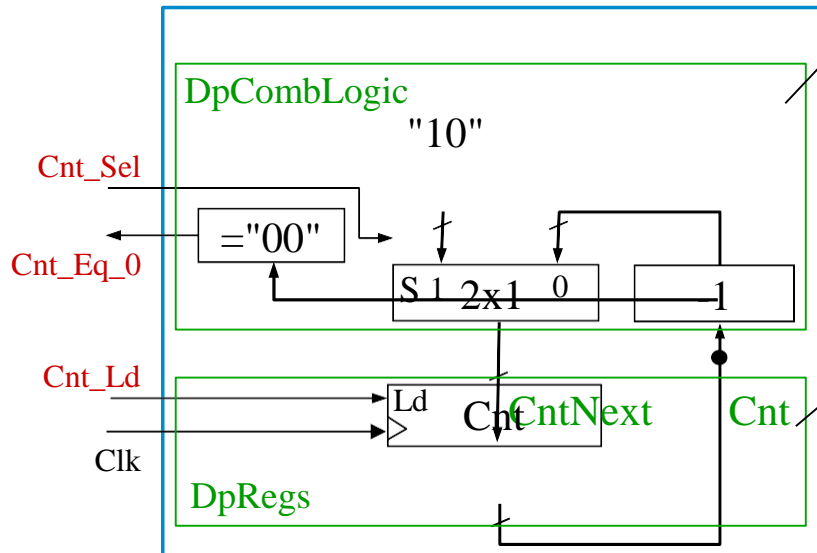- Combinational part and register part
- Current and next signals shared between the two parts
- Just like for FSM behavior



```
...
// Shared variables
reg Cnt_Eq_0, Cnt_Sel, Cnt_Ld;
// Controller variables
reg [0:0] State, StateNext;
// Datapath variables
reg [1:0] Cnt, CntNext;

// ----- Datapath Procedures ----- //
// DP CombLogic
always @(Cnt_Sel, Cnt) begin
    if (Cnt_Sel==1)
        CntNext <= 2;
    else
        CntNext <= Cnt - 1;

    Cnt_Eq_0 <= (Cnt==0)?1:0;
end

// DP Regs
always @(posedge Clk) begin
    if (Rst == 1 )
        Cnt <= 0;
    else if (Cnt_Ld==1)
        Cnt <= CntNext;
end
...
```


Note use of previously-introduced conditional operator

Describing the Controller Behaviorally

23

Standard approach for describing FSM

Two procedures

 

```

...
// ----- Controller Procedures ----- //
// Ctrl CombLogic
always @(State, Cnt_Eq_0, B) begin
  case (State)
    S_Off: begin
      X <= 0; Cnt_Sel <= 1; Cnt_Ld <= 1;
      if (B == 0)
        StateNext <= S_Off;
      else
        StateNext <= S_On;
      end
    S_On: begin
      X <= 1; Cnt_Sel <= 0; Cnt_Ld <= 1;
      if (Cnt_Eq_0 == 1)
        StateNext <= S_Off;
      else
        StateNext <= S_On;
      end
    endcase
  end

// Ctrl Regs
always @(posedge Clk) begin
  if (Rst == 1 ) begin
    State <= S_Off;
  end
  else begin
    State <= StateNext;
  end
end
end
...

```

Controller and Datapath Behavior

24


Result is one module with four procedures

Datapath procedures (2)

- Combinational logic
- Registers

Controller procedures (2)

- Combinational logic
- Registers

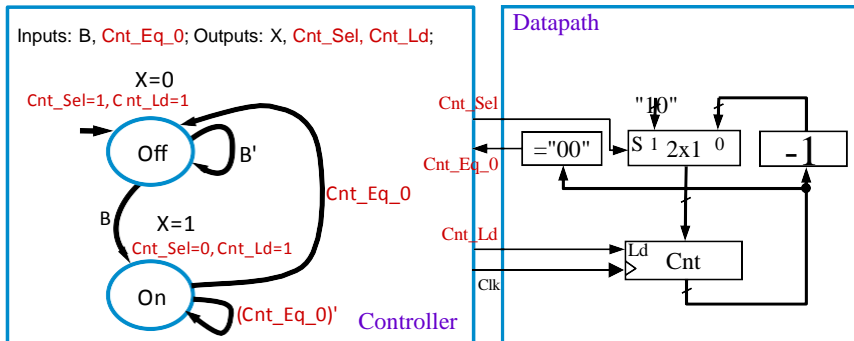

```
...
module LaserTimer(B, X, Clk, Rst);
    ...

    parameter S_Off = 0,
              S_On  = 1;

    // Shared variables
    reg Cnt_Eq_0, Cnt_Sel, Cnt_Ld;
    // Controller variables
    reg [0:0] State, StateNext;
    // Datapath variables
    reg [1:0] Cnt, CntNext;

    // ----- Datapath Procedures ----- //
    // DP CombLogic
    always @(Cnt_Sel, Cnt) begin
        ...
    end

    // DP Regs
    always @(posedge Clk) begin
        ...
    end

    // ----- Controller Procedures ----- //
    // Ctrl CombLogic
    always @(State, Cnt_Eq_0, B) begin
        ...
    end

    // Ctrl Regs
    always @(posedge Clk) begin
        ...
    end
end
endmodule
```